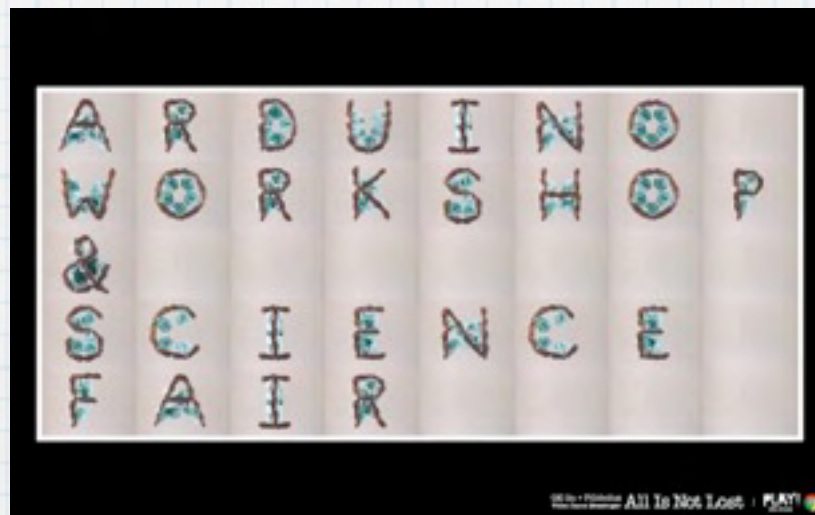


# Arduino

## Basic Electronics





# Basic Electronics

## Closed Loop System

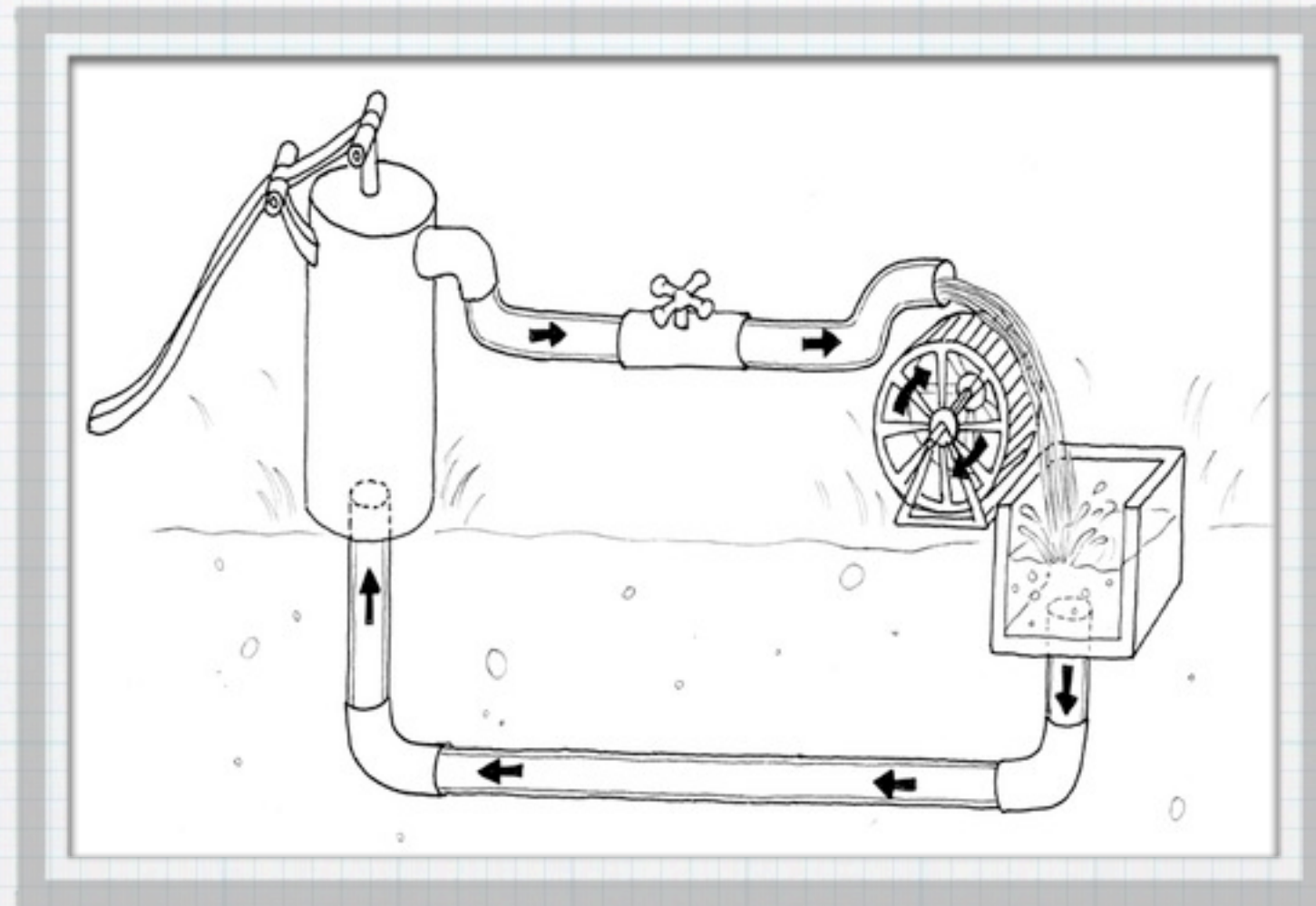


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output



Arduino


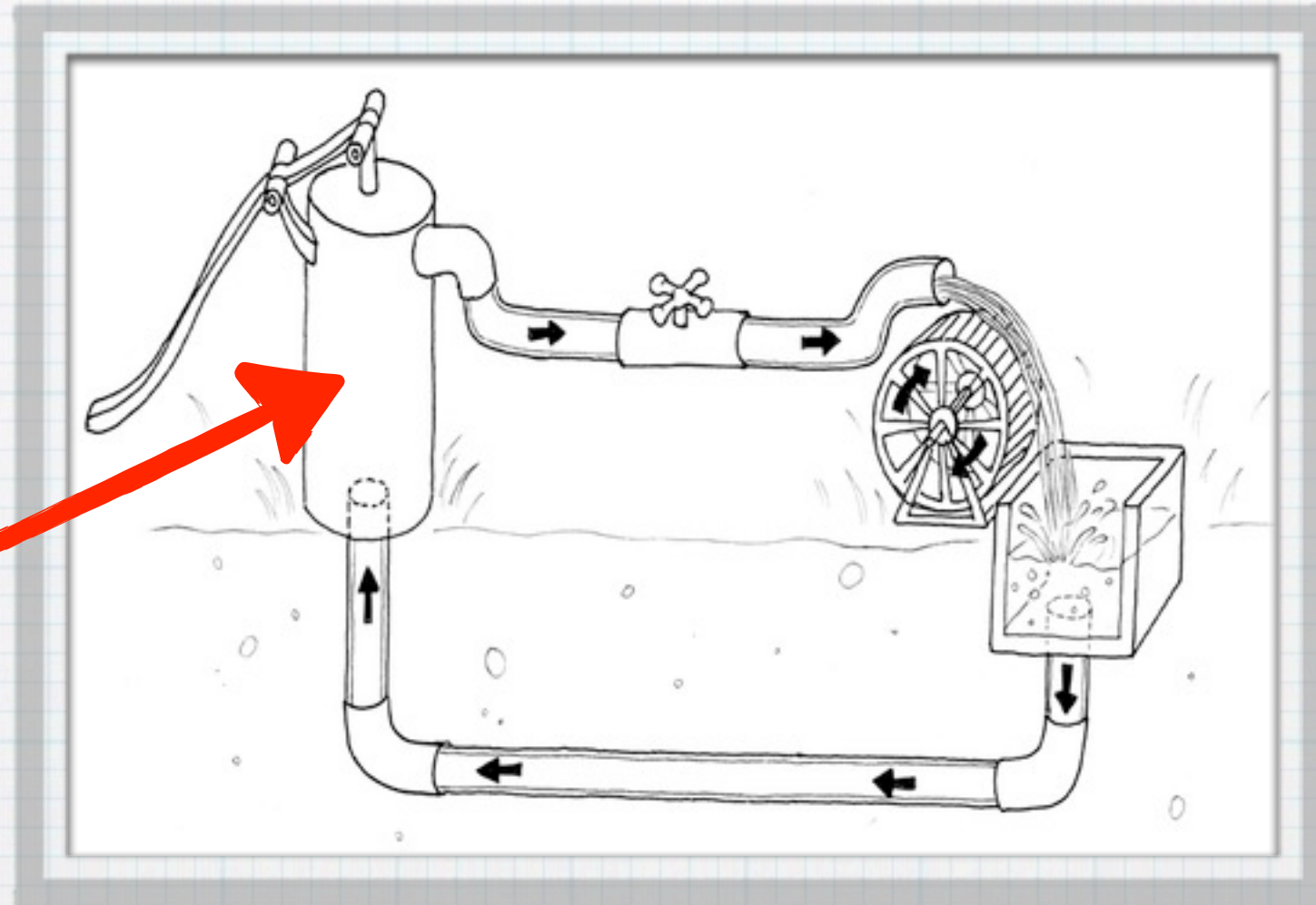


Illustration: "Getting Started with Arduino"

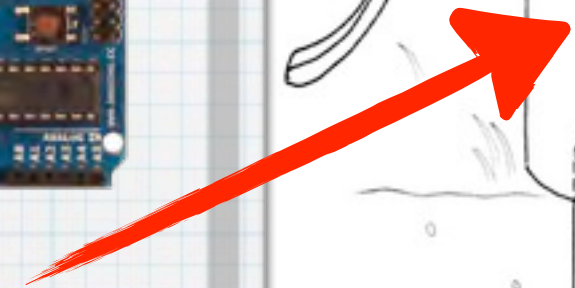

# Basic Electronics

## Digital Output

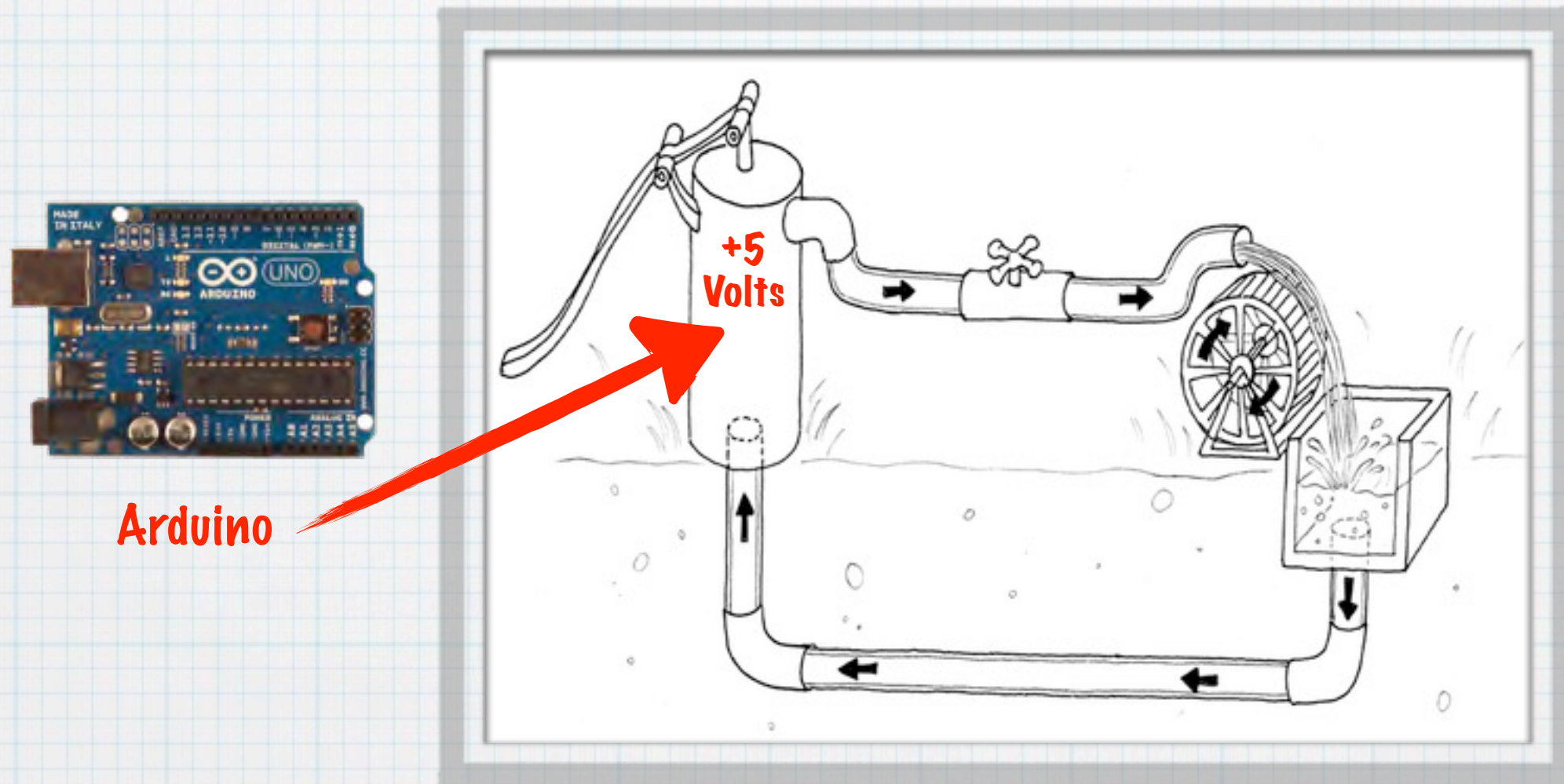


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output

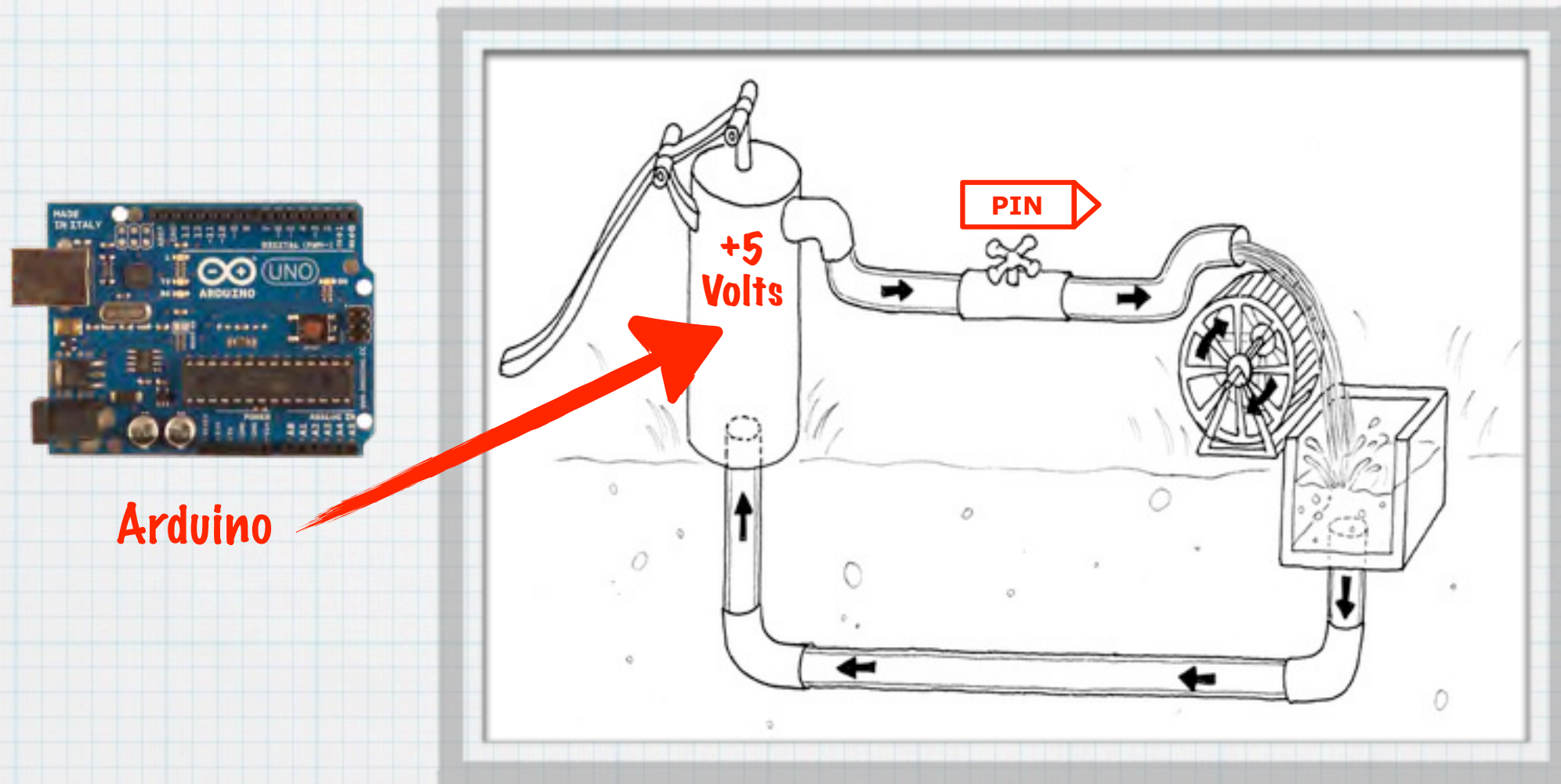


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output

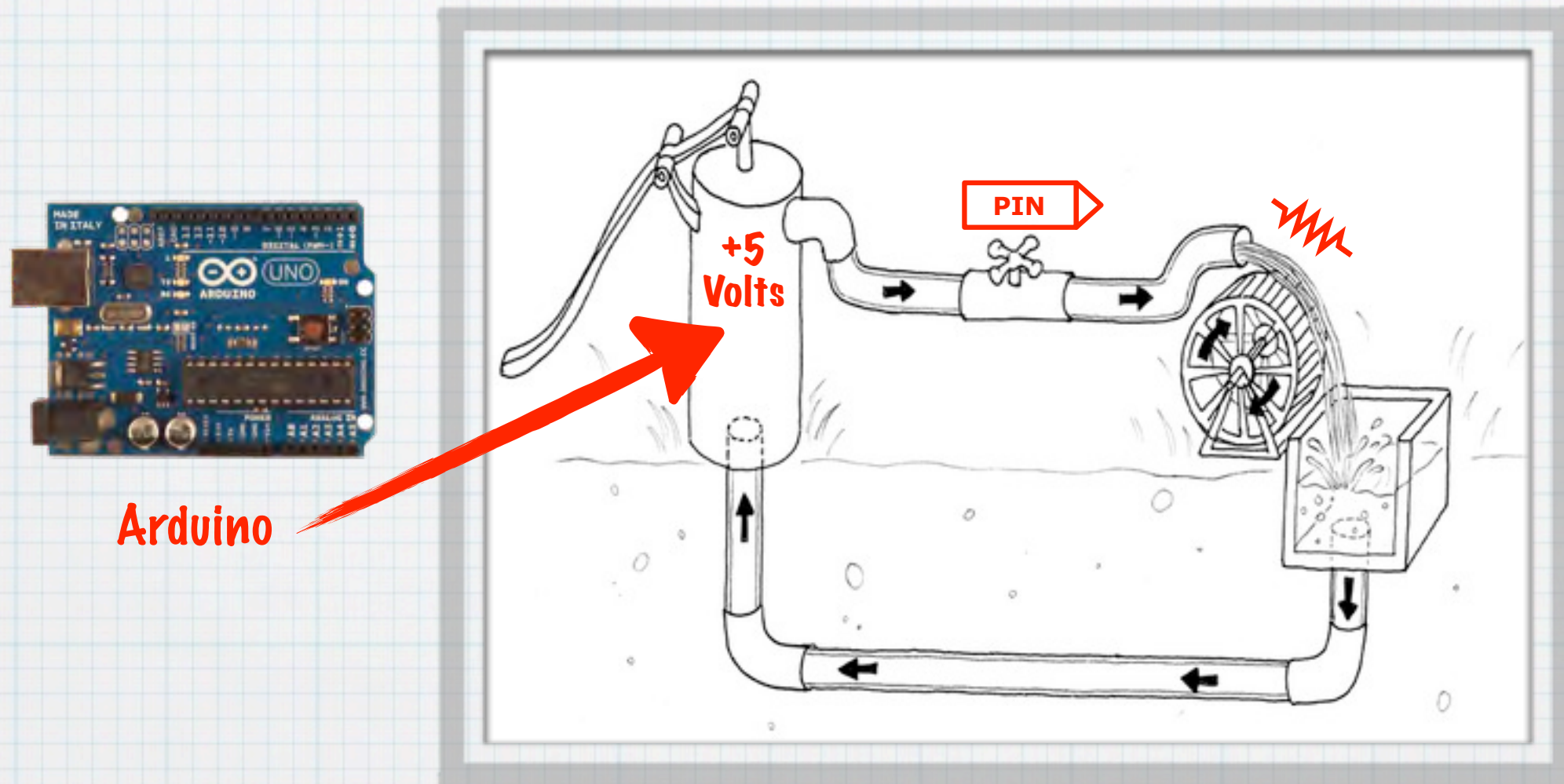


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output

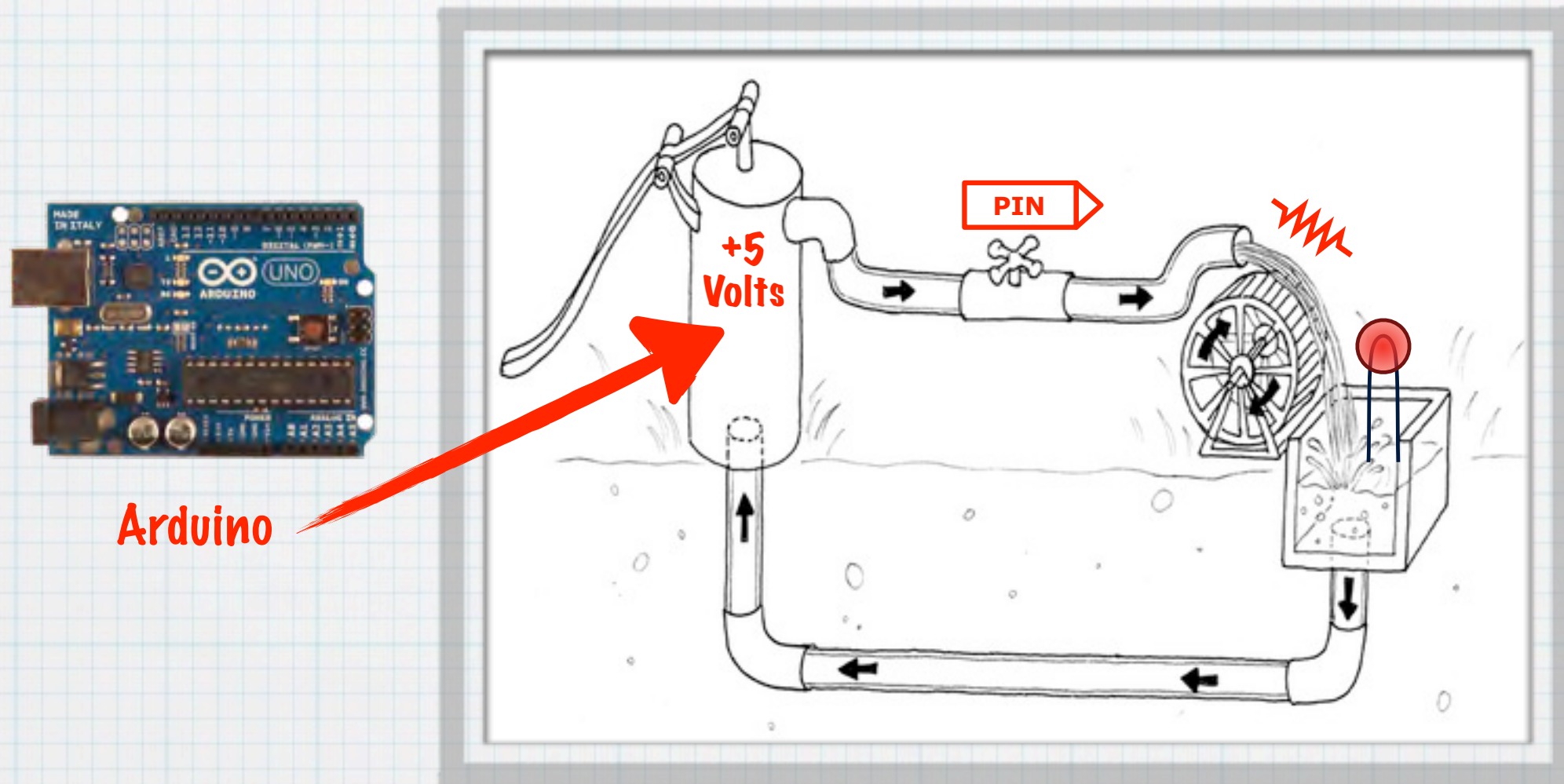


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output

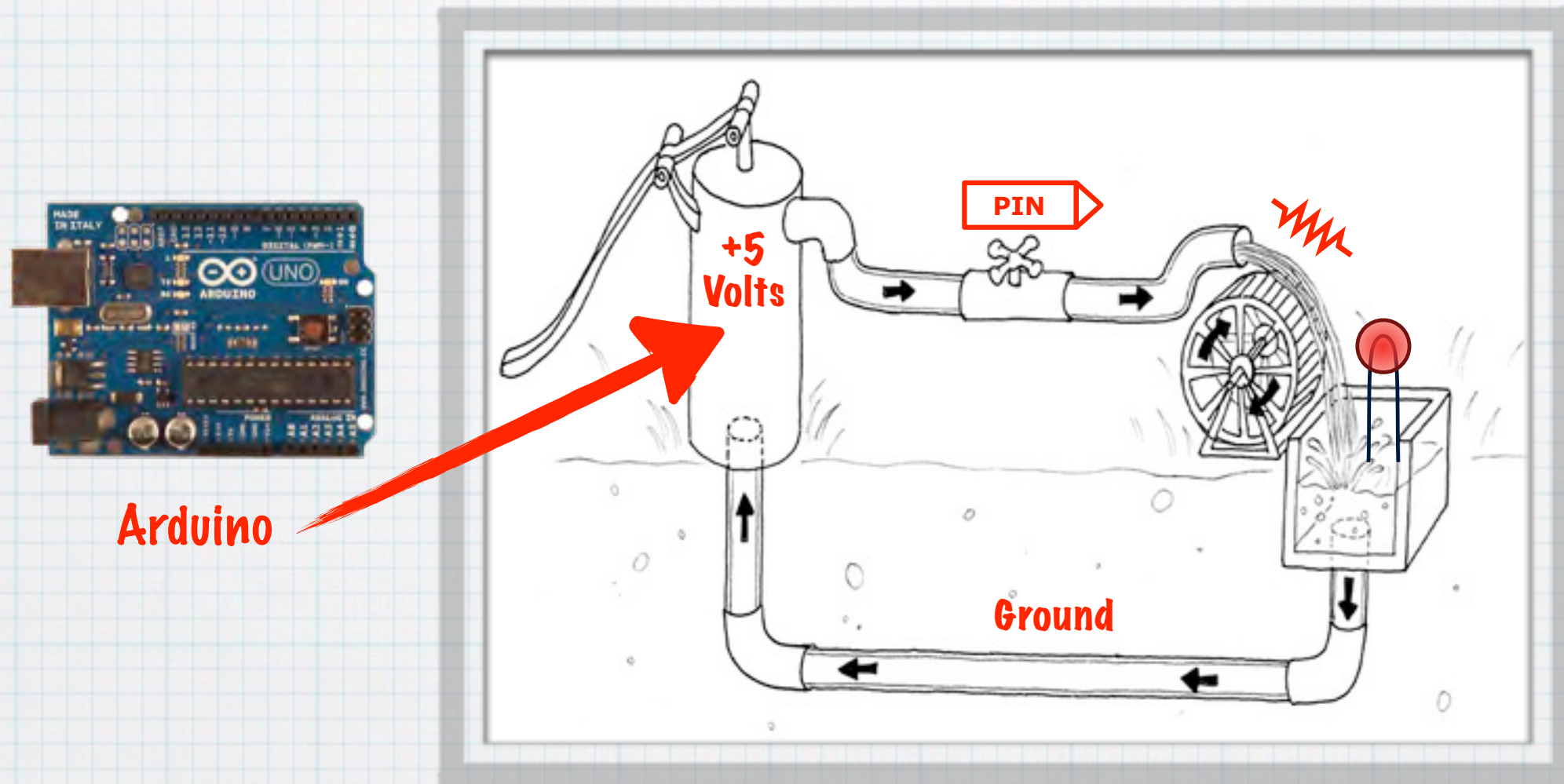


Illustration: "Getting Started with Arduino"



# Basic Electronics

## Digital Output

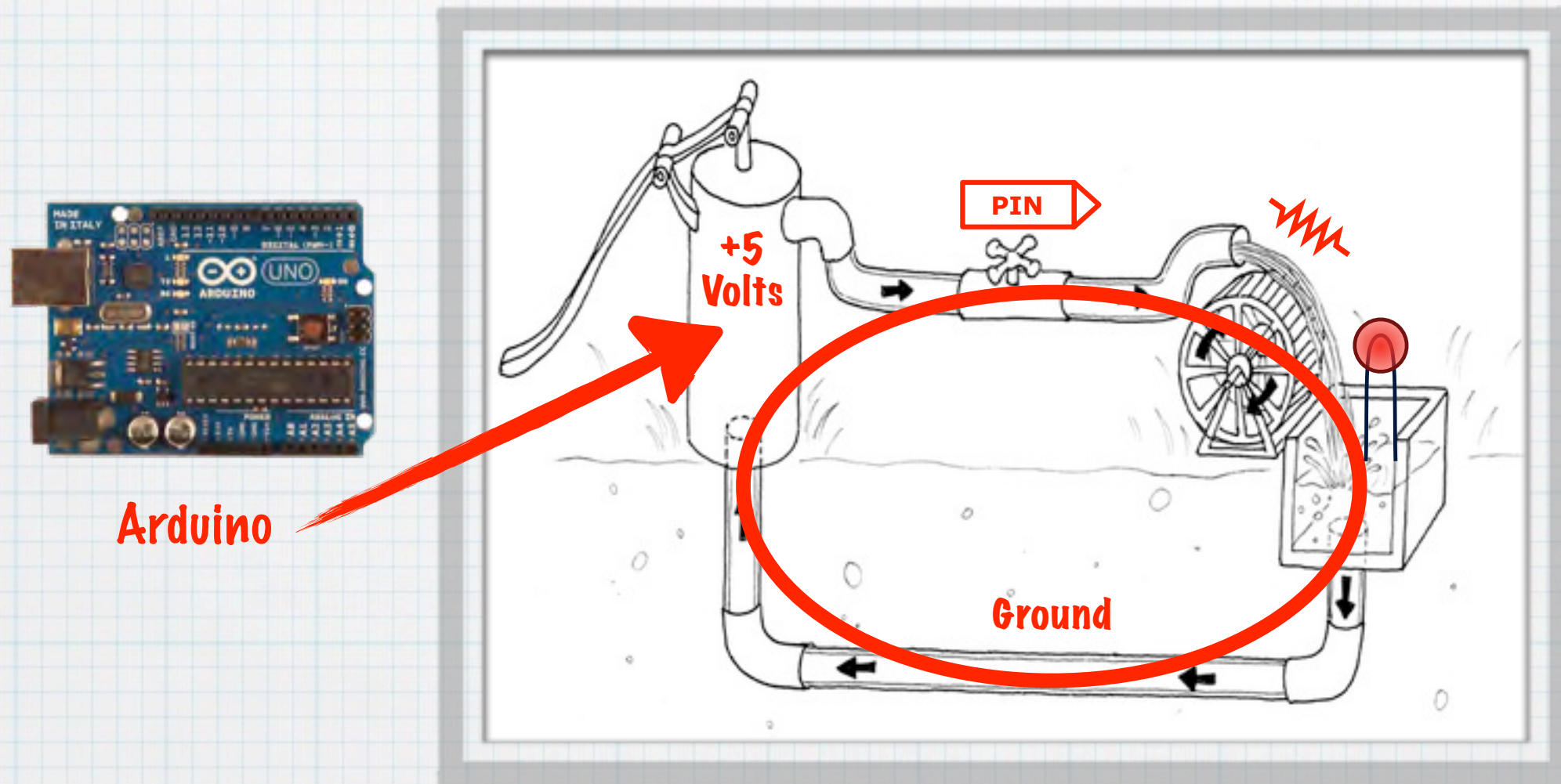


Illustration: "Getting Started with Arduino"









# Basic Electronics

## Digital Output

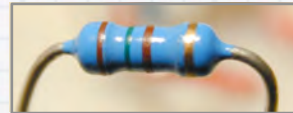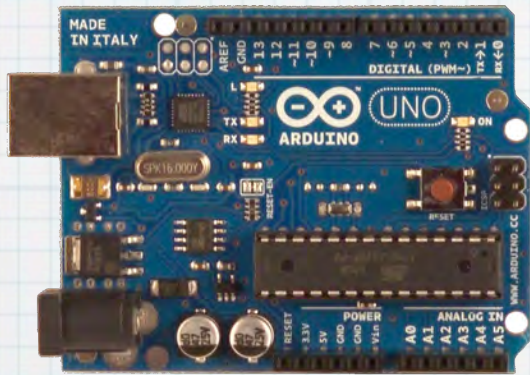

**Resistor**




**LED**



# Basic Electronics


## Digital Output

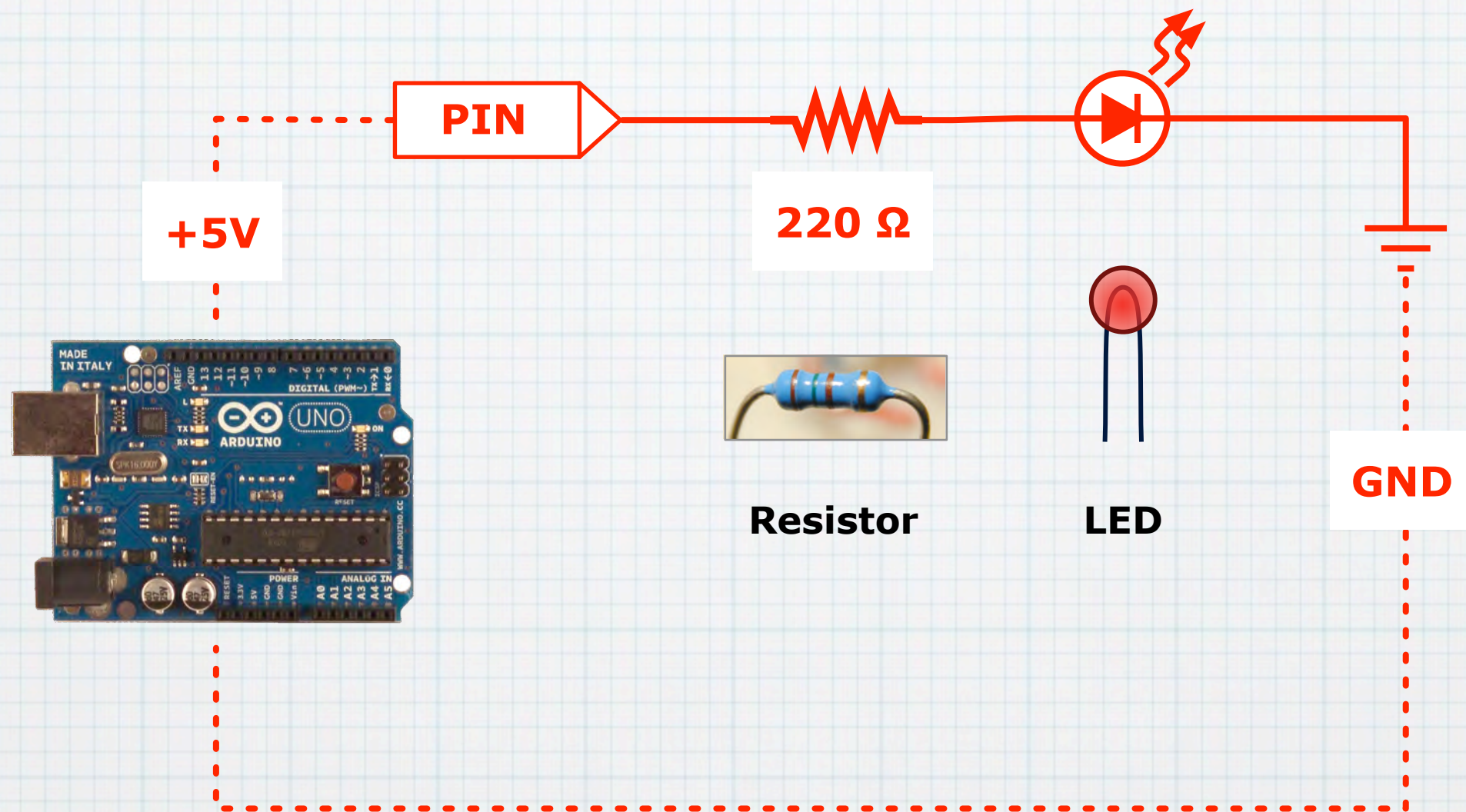



# Basic Electronics



## Digital Output

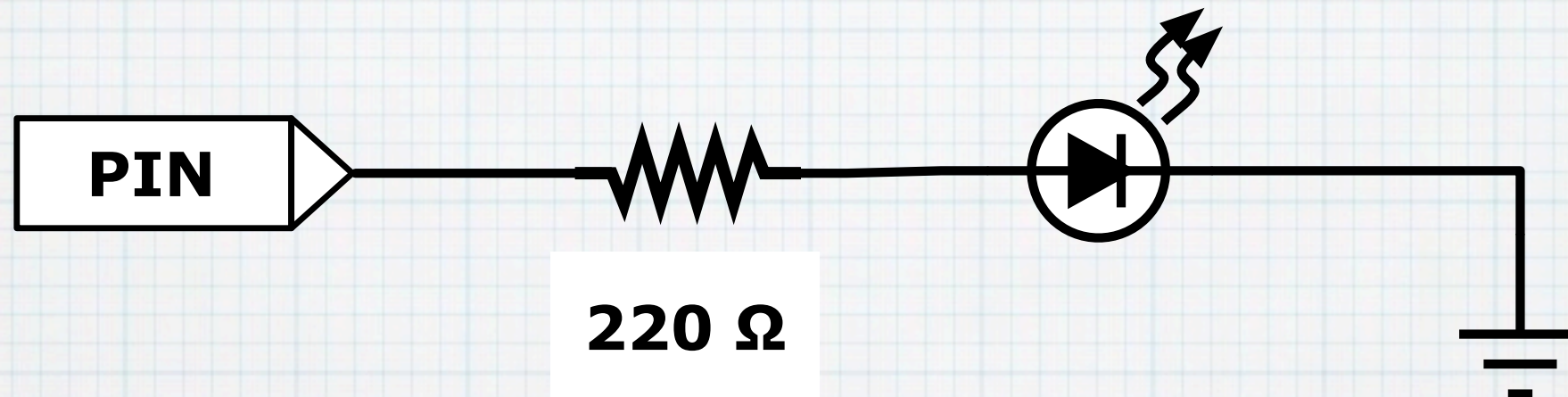



# Basic Electronics


## Digital Output

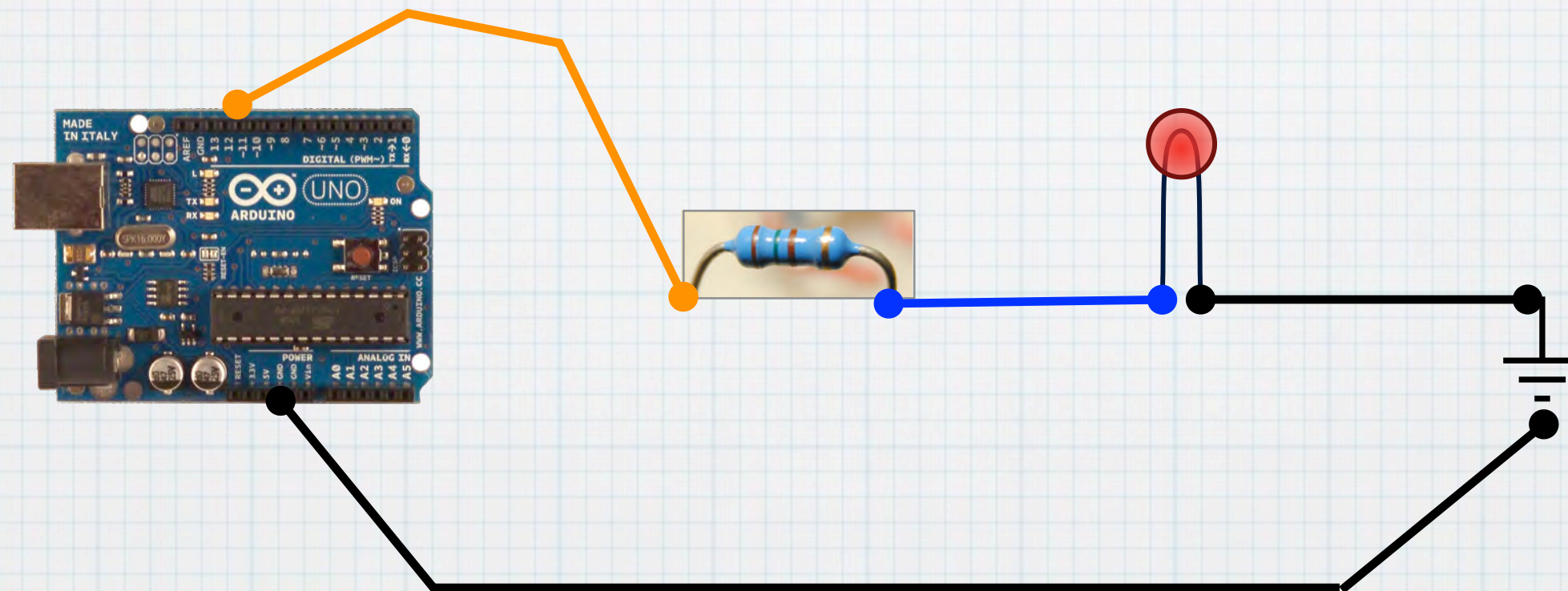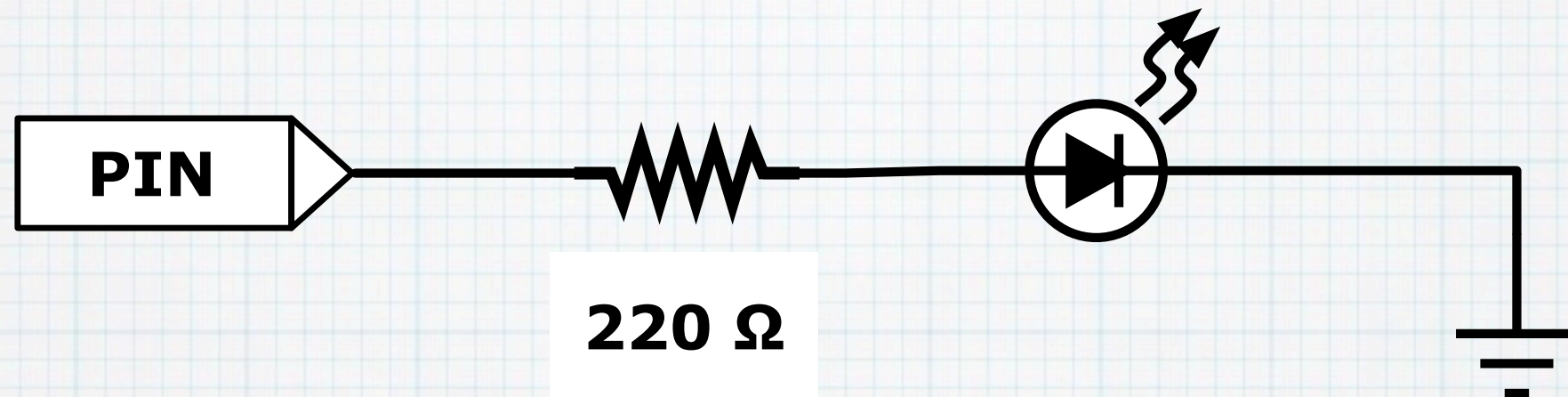



# Basic Electronics


## Digital Output

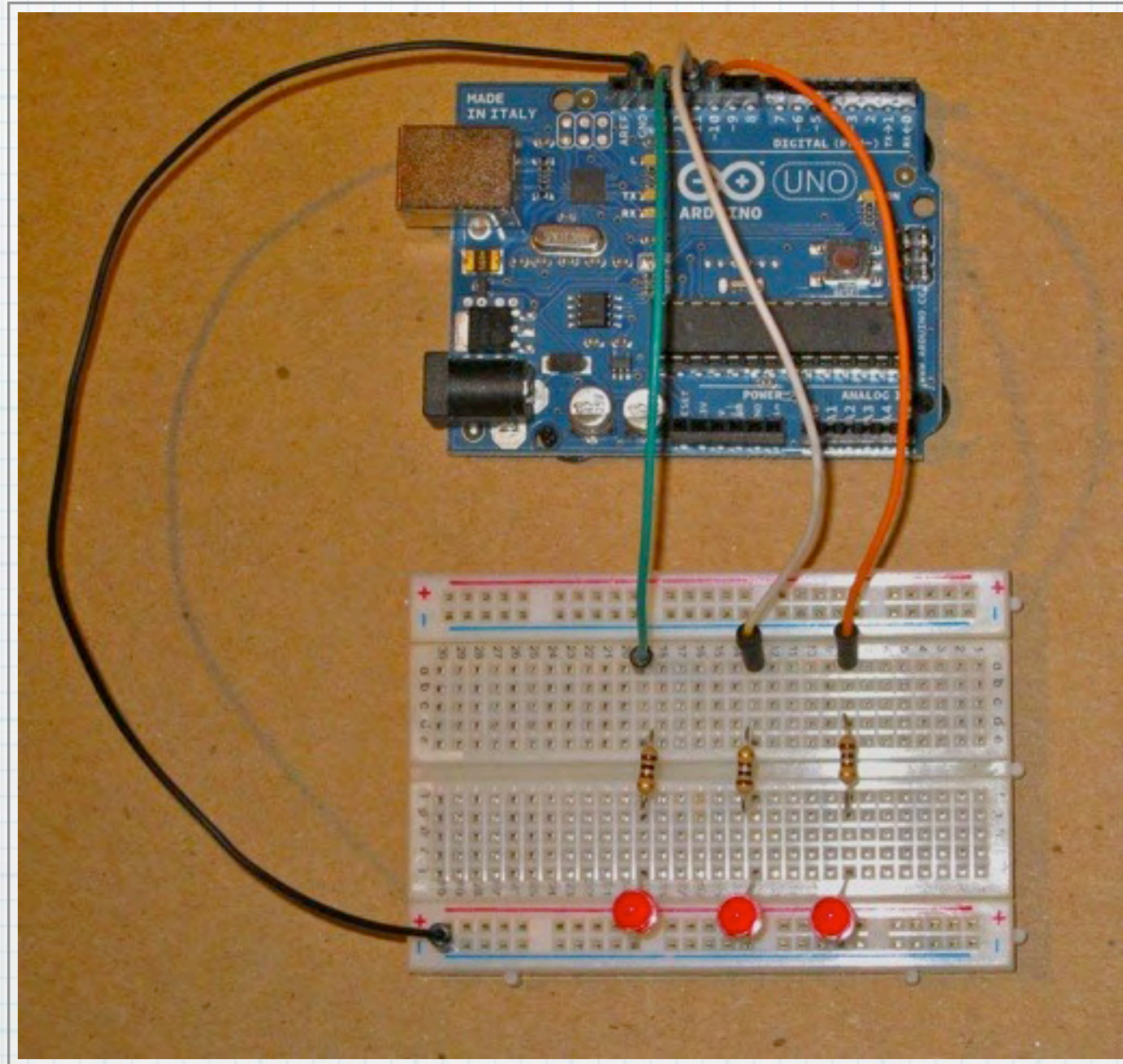



# Basic Electronics

Electrically  
Connected

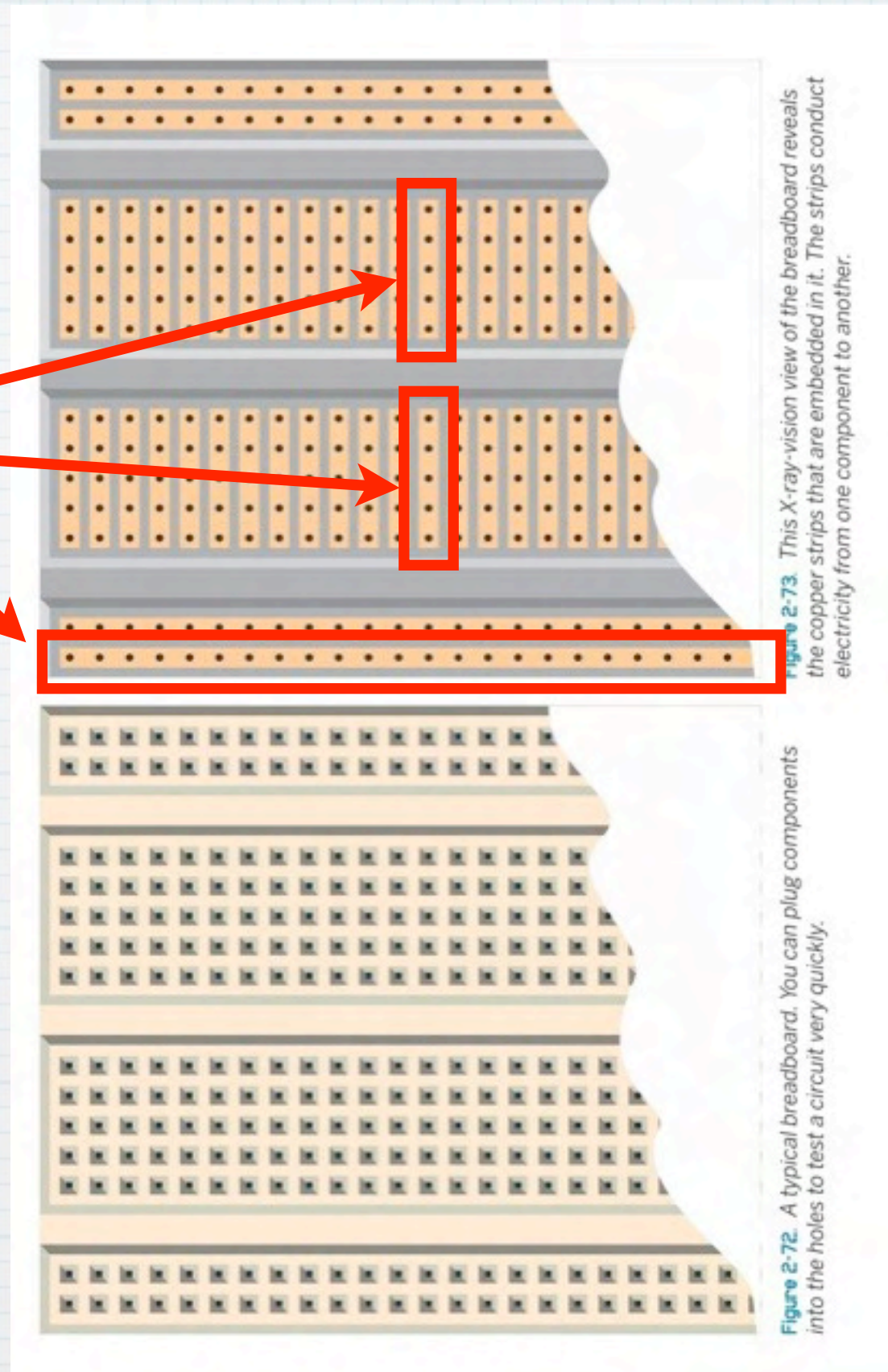



# Basic Electronics

## Digital Output

